



INTERNATIONAL INSTITUTE OF  
INFORMATION TECHNOLOGY  

---

HYDERABAD

*Department  
of  
Electronics and communication Engineering*

Analog Electronics Circuits  
Dr . Anshu Sarje

Lab: 0

Name: Macharla Harish  
Roll no: 2020102062  
Date : 23/08/2021

August 23, 2021

## 1 Objectives


- Analysing the circuit(Parallel Resistors and Current Division)theoretically and simulation using LT-spice of DC operating point and Transient Analysis.

## 2 Components used

- Voltage source.
- Three resistors.
- connecting wires.
- Ground.

## 3 Theoretical Calculation:

### 3.1 DC operating point:

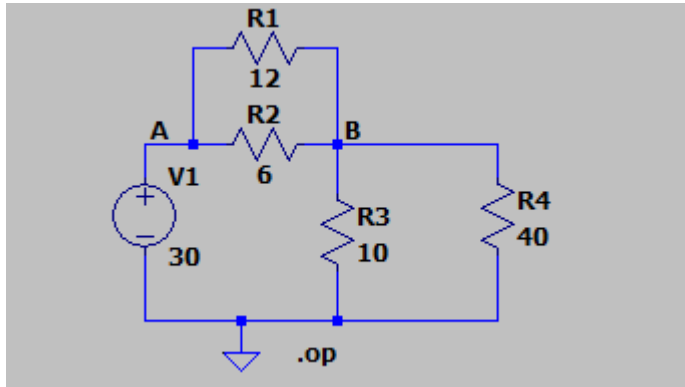

Here we can see Resistance R1 12Ω and R2 6Ω are in parallel,  $R_{result1} = 4\Omega$  and also R3 10Ω and R4 40Ω are also in parallel,  $R_{result2} = 8\Omega$ , these resultant resistances are in Series.

$R_{equivalent} = 12\Omega$ .

The current in the entire circuit

$$i = \frac{V}{R}$$
$$= \frac{30}{12} = 2.5$$

.

Voltage across  $R_{result1}$  :  $V = I \times R_{result1} = 2.5 \times 4 = 10V$ .

Current through R1:

$$= \frac{10}{12}$$
$$= 0.8333A$$

Current through R2:

$$= \frac{10}{6}$$
$$= 1.667A$$

.

Voltage across  $R_{result2}$  :  $V = I \times R_{result2} = 2.5 \times 8 = 20V$ .

Since R3 and R4 are in parallel they have same voltages.

Current through R3:

$$= \frac{20}{10}$$
$$= 2A$$

Current through R4:

$$= \frac{20}{40}$$
$$= 0.5A$$

.

## 4 Observations:

- I observed that both Theoretical and simulation in LT-spice results were same.

```


--- Operating Point ---

V(a) :      30      voltage
V(b) :      20      voltage
I(R2) :      1.66667 device_current
I(R1) :      0.833333 device_current
I(R4) :      0.5     device_current
I(R3) :      2       device_current
I(V1) :     -2.5     device_current


```
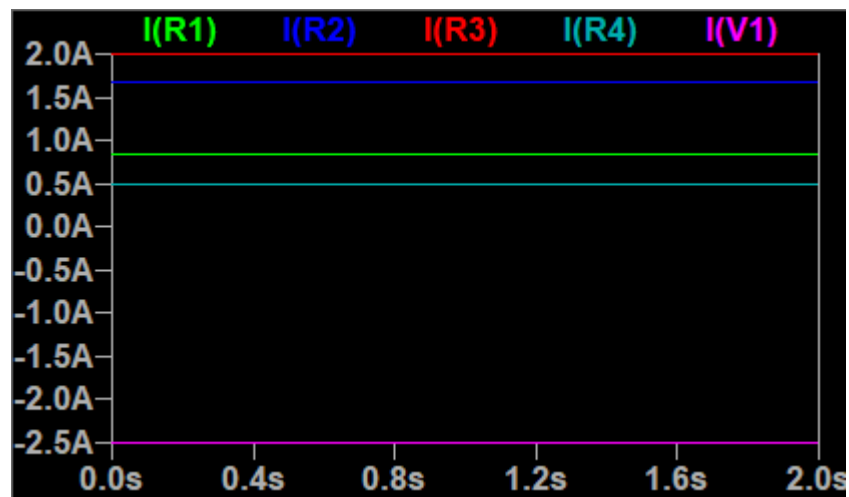
## 5 Plots


Plots of above DC operating values using Transient analysis.



Plots of current across the resistors.

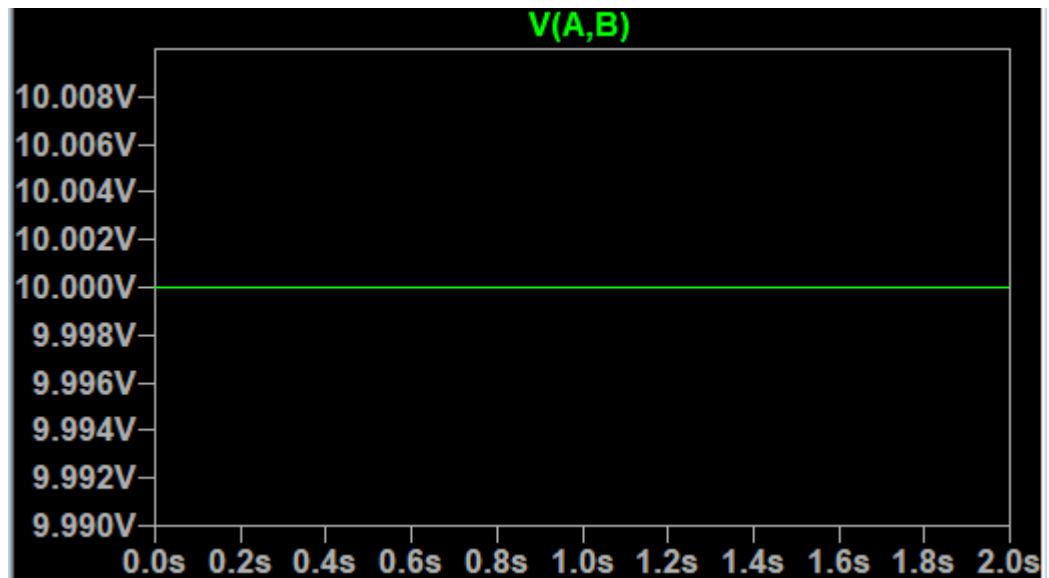

Plot of voltage drop across A and B.

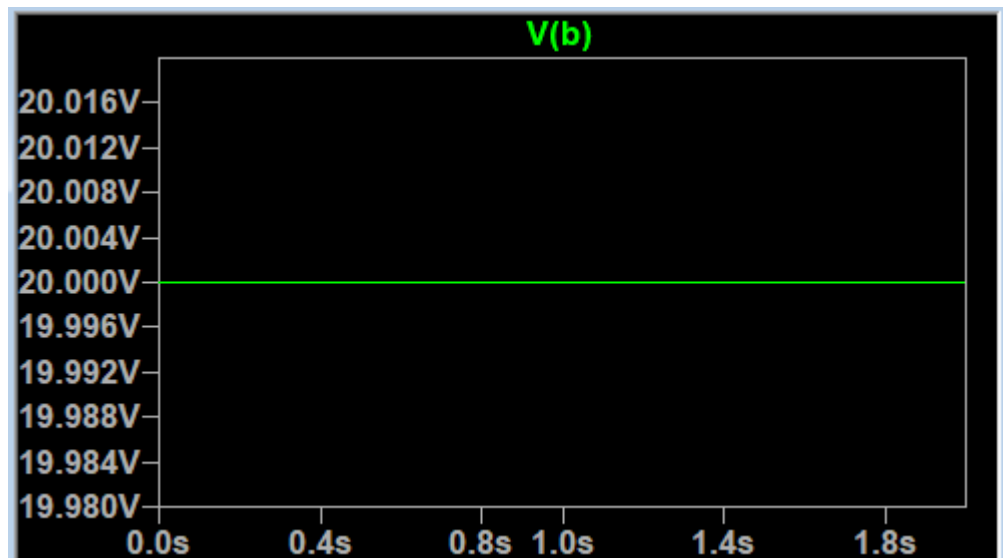

Plot of voltage drop across B and ground

## 6 Conclusion

- LT -spice is a good tool which helps us to understand the subject both theoretically and conceptually.
- I conclude that both the results DC operating values, theoretical and Transient Analysis were same.